



# Rajshahi University of Engineering & Technology

**Department of Electrical & Computer Engineering.**

## Lab report

**Course Code : ECE 1202**  
**Course Title : Circuits and System-II Sessional**  
**Date of Experiment :10/09/2024**  
**Date of Submission :10/09/2024**

Submitted To:	Submitted By:
<b>Oishi Jyoti</b> <b>Assistant Professor</b> <b>Department of ECE, RUET</b>	<b>Name : Shadman Zaman</b> <b>Roll : 2210018</b> <b>Registration : 1072</b> <b>Session : 2022-2023</b> <b>Department of ECE, RUET</b>

## Experiment No. 03

**Experiment Name:** Power Measurement of a Balanced 3-Phase System Using the Two Wattmeter Method.

### Objective:

To understand and analyze the measurement of power in a balanced three-phase system using the two-wattmeter method and verify the theoretical relationships experimentally.

### Theory:

In a three-phase electrical system, power measurement can be achieved using the two-wattmeter method, especially in balanced and unbalanced loads. The two-wattmeter method uses two wattmeters connected in a way that they can measure power even if the system is unbalanced. The total power in a balanced three-phase system is the sum of the readings of the two wattmeters.

- **Wattmeter Readings (P1 and P2):**

These measure power delivered to the load from two different lines of the three-phase system.


- **Total Power (P):**

The total power delivered to the load in a balanced system can be calculated by adding the readings of the two wattmeters:  $P = P_1 + P_2$ .

### Required Apparatus:

- Three-phase AC power supply.
- Balanced three-phase load (resistors).
- Two wattmeters.
- Voltmeter.
- Ammeter.
- Connecting wires.
- VARIAC.
- Multimeter.

### Circuit Diagram:

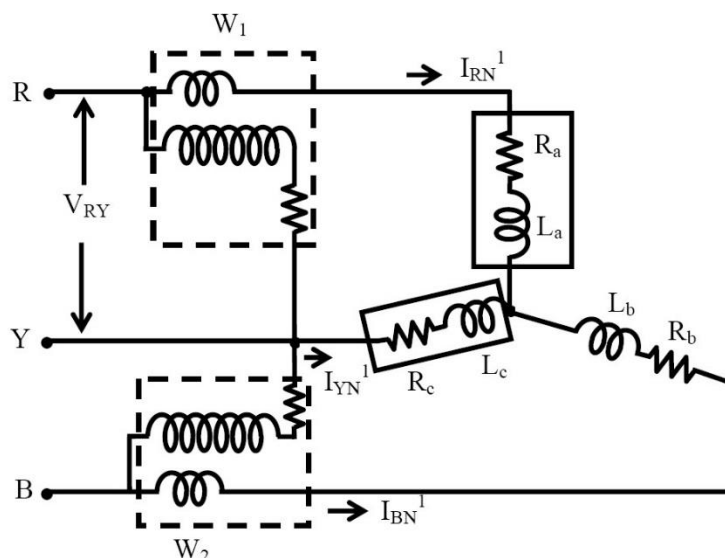

**Procedure:**

1. Set up the circuit with two wattmeters connected as per the two-wattmeter method configuration for three-phase power measurement.
2. Ensure that the load is connected in a balanced three-phase configuration.
3. Apply the three-phase voltage using the AC power supply and gradually increase it using the VARIAC.
4. Record the readings of both wattmeters (P1 and P2).
5. Measure the line voltage (V\_Line) and the line current (I\_Line) using the voltmeter and ammeter, respectively.
6. Calculate the total power using the sum of the two wattmeter readings

Data Table:

Serial No	P <sub>1</sub>	P <sub>2</sub>	P <sub>T(m)</sub> (P <sub>1</sub> +P <sub>2</sub> )	P <sub>T(c)</sub> = $\sqrt{3}$ V <sub>L</sub> I <sub>L</sub>	V <sub>L</sub>	I <sub>L</sub>	Error = $ (P_{Tc}-P_{Tm})/P_{Tm} $ *100%
1	40	40	80	97	87	.65	21.25
2	20	20	40	52.79	63.5	.42	31.6
3	30	30	60	71.7	74	.56	19.5
4	36	36	72	91.2	74	.62	26.67
5	64	64	128	176	105.2	.97	37.5

**Result:** The experimental measurements show that the total power calculated using the two-wattmeter method closely matches the expected values based on the theoretical calculations. The minor errors observed can be attributed to measurement inaccuracies, losses in the circuit, or external factors.

**Discussion:** Ignoring the small margin of errors which may have caused due to internal or external factors, the experiment was a success.

Data table from actual lab experiment:

Exp. name: Power measurement of a balanced 3- $\phi$  system using two wattmeter method

SL	$P_1$	$P_2$	$P_T (m)$ $[P_1 + P_2]$	$P_T (W)$ $= \sqrt{3} V_L I_L$	$V_L$	$I_L$	Error $= \left  \frac{P_T - P_{Tm}}{P_{Tm}} \right  \times 100$
1	40	40	80	97	87	0.65	21.25
2	20	20	40	52.79	63.5	0.48	31.9
3	30	30	60	71.7	74	0.56	19.5
4	36	36	72	91.2	85	0.62	26.67
5	64	64	128	176	105.2	0.97	37.5

Roll: 2210013  
2210014

~~2210015~~

2210016

2210017

2210018

2210020

2210021

2210023

  
10.09.24