

*Heaven's Light is Our Guide*



# Rajshahi University of Engineering & Technology

**Department of Electrical & Computer Engineering**

## Lab Report

Experiment No: 02

Name of the experiment: Study the relationship between phase & line current & voltage of a Delta ( $\Delta$ ) connected three-phase balanced system.

Course Code	1202
Course Title	Circuit & System – II Sessional

Submitted By:	Submitted To:
Name : Sharmin Akter	Oishi Jyoti, Lecturer. Electrical & Computer Engineering, RUET.
Roll : 2210055	
Registration : 1109	
Session : 2022-23	

# INDEX

1. Experiment No
2. Experiment Name
3. Objectives
4. Required Apparatus
5. Theory
6. Circuit Diagram
7. Procedure
8. Data Table
9. Result
10. Discussion

## Experiment No: 01

**Name of the Experiment:** Study the relationship between phase & line current & voltage of a Delta ( $\Delta$ ) connected three-phase balanced system.

### Objectives:

- To learn how to make Delta ( $\Delta$ ) connections
- To study the relationship between voltage & current in three-phase system

### Required Apparatus:

- Voltmeter
- AC Voltage source
- Ammeter
- Connecting wires
- Resistors


**Theory:** In a Delta ( $\Delta$ ) connected three-phase system, the line and phase quantities are related by,

$$V_p = V_L$$

$$I_p = I_L/\sqrt{3}$$

Where  $V_p$  is phase voltage,  $V_L$  line voltage.  $I_L$  &  $I_p$  are line current & phase current respectively.

### Circuit Diagram:

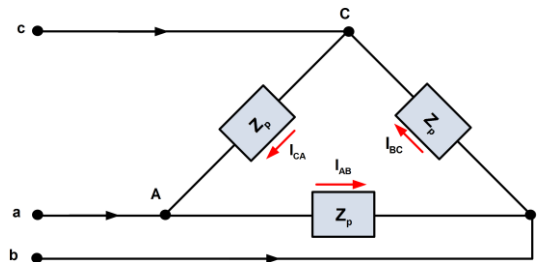

### Procedure:

- A circuit was created following the circuit diagram using the components required.
- Voltmeter and ammeter were connected in the places marked in the diagram.
- Readings of the meters were recorded in a data table and error was calculated.

### Calculations:

Delta Connection,  $V_p = V_L$ ; finding errors for  $I_L$  &  $I_p$

For 1,

$$I_p(c) = 1.5/\sqrt{3} = 0.86$$

$$\begin{aligned}\text{Error} &= (0.86 - 0.8)/0.86 \\ &= 6.97\%\end{aligned}$$

For 2,

$$I_p(c) = 2.3/\sqrt{3} = 1.32$$

$$\text{Error} = (1.32-1.2)/1.32 \\ = 9.09\%$$

For 3,

$$I_p(c) = 3.8/\sqrt{3} = 2.19$$

$$\text{Error} = (2.19-2.1)/2.19 \\ = 4.11\%$$

For 4,

$$I_p(c) = 4.3/\sqrt{3} = 2.48$$

$$\text{Error} = (2.48-2.3)/2.48 \\ = 7.26\%$$

#### Data Table:

SI	$I_L$	$I_p(m)$	$I_p(c)$	$V_L$	$V_p$	Error
1	1.5	0.8	0.86	40	40	6.97%
2	2.3	1.2	1.32	60	60	9.09%
3	3.8	2.1	2.19	80	80	4.11%
4	4.3	2.3	2.48	100	100	7.26%

Data Table:

Roll :

SI	$I_L$	$I_{p_m}$	$I_{p_c}$	$V_p$	$V_L$	%
1	1.5	0.8	0.86	40	40	6.97
2	2.3	1.2	1.32	60	60	9.09
3	3.8	2.1	2.19	80	80	4.11
4	4.3	2.3	2.48	100	100	7.26

2210055  
2210056  
2210057  
2210058  
2210059  
2210060  
2210061

22100524

#### Result:

The measured line and phase voltages are the same as it was a Delta ( $\Delta$ ) connection. But the relation between line and phase current is -  $I_p = I_L/\sqrt{3}$  as it can be seen from the calculations.

#### Discussion:

Ignoring the small margin of error, the experiment proved the theory. Error could have been avoided but due to some external & internal factors it was unavoidable.

