

Heaven's Light is Our Guide

Rajshahi University of Engineering & Technology

Department of Electrical & Computer Engineering

Lab report

Course Code : ECE 1202

Course Title : Circuits & Systems-II Sessional

Date of experiment : 04- 06- 2024

Date of Submission : 10- 09- 2024

Submitted To:	Submitted By:
Oishi Jyoti Assistant Professor, Department of ECE, RUET	Name : Md. Naimur Rahman Naim Roll : 2210026 Registration : 1080 Session : 2022-2023 Department of ECE, RUET

Experiment no.: 02

Experiment name: Study the relationship between phase current & line current of a delta connected 3-phase balanced system.

Theory: In a balanced 3 – ϕ Y - Δ system, phase currents are:

$$I_{ab} = \frac{V_{ab}}{Z_{\Delta}}, I_{bc} = \frac{V_{bc}}{Z_{\Delta}} \text{ and } I_{ca} = \frac{V_{ca}}{Z_{\Delta}}$$

The line currents can be obtained from applying KCL. So, the line currents will be:

$$I_A = I_{ab} - I_{ca}, I_B = I_{bc} - I_{ab} \text{ and } I_C = I_{ca} - I_{bc}$$

Since, $I_{CA} = I_{AB} \angle -240^\circ$,

$$I_A = I_{ab} - I_{ca} = I_{ab} (1 - 1 \angle -240^\circ) = I_{ab} (1 + 0.5 - j0.866) = I_{ab} \sqrt{3} \angle 30^\circ$$

Now, if we consider the magnitude only, we get the relation between phase and line current as,

$$I_P = \frac{I_L}{\sqrt{3}} \dots \dots \dots (1)$$

Required Apparatus:

1. Source
2. VARIAC
3. Voltmeter
4. Ammeter
5. Resistor
6. Multimeter
7. Connecting wires

Circuit diagram:

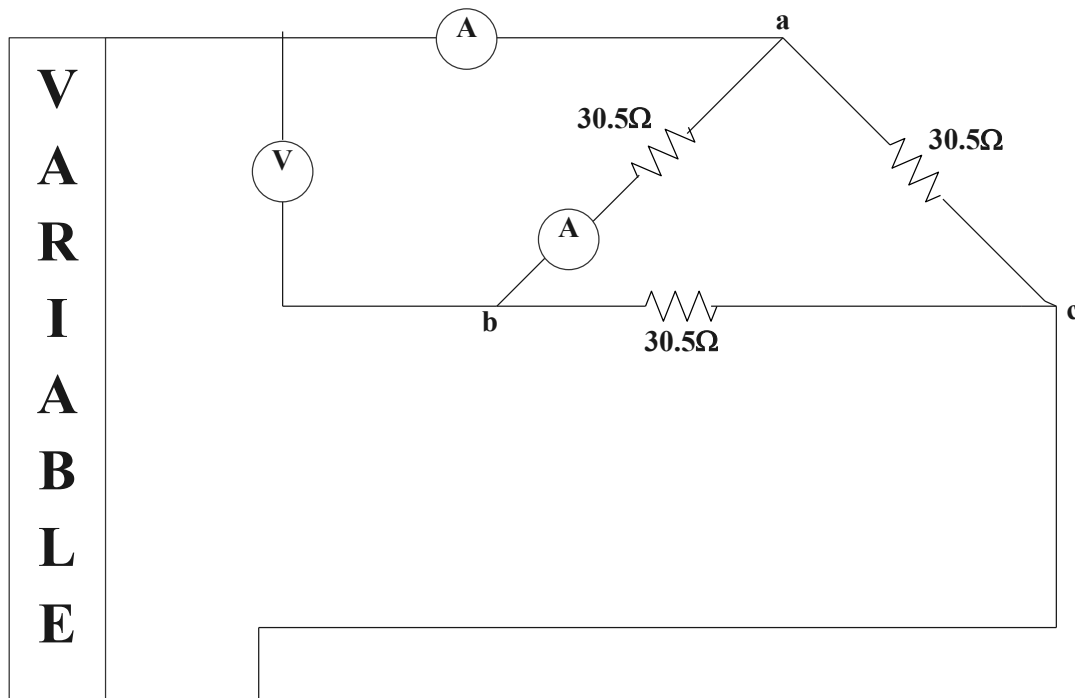


Fig. : Delta connected 3-phase balanced circuit

Calculation:

- **Reading 1:**

Line current, $I_L = 2.25 \text{ A}$

Measured phase current, $I_{P(m)} = 1.26 \text{ A}$

Calculated phase current, $I_{P(calc)} = 1.29 \text{ A}$

$$\text{Error} = \frac{|I_{P(calc)} - I_{P(m)}|}{I_{P(calc)}} \times 100\% = \frac{|1.29 - 1.26|}{1.29} \times 100\% = 2.32\%$$

- **Reading 2:**

Line current, $I_L = 0.72 \text{ A}$

Measured phase current, $I_{P(m)} = 0.39 \text{ A}$

Calculated phase current, $I_{P(calc)} = 0.41 \text{ A}$

$$\text{Error} = \frac{|I_{P(calc)} - I_{P(m)}|}{I_{P(calc)}} \times 100\% = \frac{|0.41 - 0.39|}{0.41} \times 100\% = 4.87\%$$

- **Reading 3:**

Line current, $I_L = 1.28 \text{ A}$

Measured phase current, $I_{P(m)} = 0.7 \text{ A}$

Calculated phase current, $I_{P(\text{calc})} = 0.74 \text{ A}$

$$\text{Error} = \frac{|I_{P(\text{calc})} - I_{P(\text{m})}|}{I_{P(\text{calc})}} \times 100\% = \frac{|0.74 - 0.7|}{0.74} \times 100\% = 5.4\%$$

- **Reading 4:**

Line current, $I_L = 1.87 \text{ A}$

Measured phase current, $I_{P(\text{m})} = 1.04 \text{ A}$

Calculated phase current, $I_{P(\text{calc})} = 1.08 \text{ A}$

$$\text{Error} = \frac{|I_{P(\text{calc})} - I_{P(\text{m})}|}{I_{P(\text{calc})}} \times 100\% = \frac{|1.08 - 1.04|}{1.08} \times 100\% = 3.7\%$$

- **Reading 5:**

Line current, $I_L = 2.79 \text{ A}$

Measured phase current, $I_{P(\text{m})} = 1.59 \text{ A}$

Calculated phase current, $I_{P(\text{calc})} = 1.61 \text{ A}$

$$\text{Error} = \frac{|I_{P(\text{calc})} - I_{P(\text{m})}|}{I_{P(\text{calc})}} \times 100\% = \frac{|1.61 - 1.59|}{1.61} \times 100\% = 1.24\%$$

$$\therefore \text{Average error} = \frac{2.32 + 4.87 + 5.4 + 3.7 + 1.24}{5} = 3.506\%$$

Table for Studying Relation Between Line and Phase Voltage:

Serial No	Line Current, I_L (A)	Measured Phase Current, $I_{P(\text{m})}$ (A)	Calculated Phase Current, $I_{P(\text{calc})}$ (A)	Percentage of Error (%)	Line Voltage, V_L (V)	Phase Voltage, V_P (V)
1	41.47	23.5	24.07	2.32	39.0	38.3
2	34.1	19	19.69	4.87	12.84	12.83
3	55.5	31.4	32.04	5.4	22.15	21.83
4	63.6	35.6	36.72	3.7	32.17	31.6
5	71.7	40.5	41.4	1.24	47.3	47.1

Result: Average percentage of error was 3.506%

Discussion: Through the experiment, we proved the relation between phase and line current in a 3 – ϕ balanced Y - Δ system. After all the calculations, we figured our error margin was 3.506% which is negligible. This little error margin certifies that, the line current is $\sqrt{3}$ times that of phase current.

Reference:

Fundamentals of Electric Circuits by Charles K. Alexander and Mathew N. O. Sadiku.