

"Heaven's Light is Our Guide"

Rajshahi University of Engineering & Technology  
Rajshahi, Bangladesh



Department of Electrical & Computer Engineering

Course Code: ECE 1205

Course Title: Circuits and systems Sessional-II

## LAB REPORT-2

Date of Submission: 07-10-2024

Submitted by  
A.H.M Moynul Kabir  
Roll No. 2210023  
Reg No. 1077/2022-2023  
Rajshahi University of  
Engineering and Technology

Submitted to  
Oishi Jyoti  
Assistant professor  
Department of ECE  
Rajshahi University of  
Engineering & Technology

## Experiment No :3

### Experiment Name: Power measurement of a balanced 3 phase system using two wattmeter method.

#### Objective:

- To examine and determine the power of the line using two wattmeter and see if it is according to the calculated value.

#### Theory:

The two-wattmeter method can be used to measure the power in a balanced three-phase system. In this case, the total power is the sum of the individual wattmeter readings. Again the calculated power can be measured from the relation,

$$P = \sqrt{3}I_L V_L$$

#### Diagram:

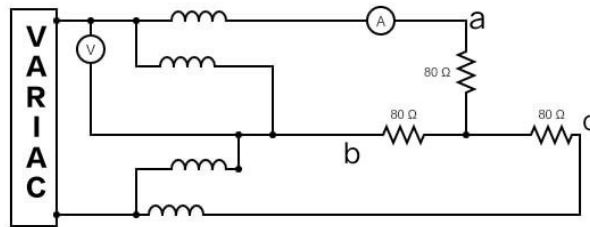


Fig.1: Two wattmeter connection of a 3-phase system.

#### Required Apparatus:

- 1.Source
2. Ammeter
- 3.Resistor (Three)
- 4.Connecting Wire
- 5.Multimeter
- 6.Two wattmeters

#### Data Table:

SL	$I_L$	$V_L$	$P_1$	$P_2$	$P_T(\text{Experiment})$	$P_T(\text{Calculated})$	Error
1	0.65	87	40	40	80	97	21.25%
2	0.48	63.5	20	20	40	52.8	31.9%
3	0.56	74	30	30	60	71.7	19.5%
4	0.62	85	36	36	72	91.2	26.67%
5	0.97	105.2	64	64	128	176	37.5%

Exp. name: Power measurement of a balanced 3- $\phi$  system using two wattmeter method

S.L	$P_1$	$P_2$	$P_T (m)$ ( $P_1 + P_2$ )	$P_T (W)$ $= \sqrt{3} V_L I_L$	$V_L$	$I_L$	Error $= \frac{P_T (m) - P_T (W)}{P_T (m)} \times 100$
1	40	40	80	97	87	0.65	21.25
2	20	20	40	52.79	635	0.93	31.9
3	30	30	60	71.7	74	0.56	19.5
4	36	36	72	91.2	83	0.62	26.67
5	64	64	128	176	105.2	0.97	37.5

Roll: 2210013  
2210014  
~~2210015~~  
2210016  
2210017  
2210018  
2210019  
2210020  
2210021  
2210022  
2210023

10.09.24

Fig.2: Table from lab

### Calculation:

Power,  $P = \sqrt{3} I_L V_L$

$$\text{Error} = \frac{21.25\% + 31.9\% + 19.5\% + 26.67\% + 37.5\%}{5} = 27.364\%$$

### Result:

The power calculated and obtained from the experiment vary from each other. The error for this experiment is 27.364% which is a big percentage. It may be caused due to the low efficiency of the component used.