

*Heaven's Light is Our Guide*

## **Rajshahi University of Engineering & Technology**



### **Course Title**

**Circuit and System -II Sessional**

**Course No : ECE 1202**

**Lab Report No : 02**

**Date of Submission :16-09-2024**

**Experiment No : 02**

**Experiment Nme :**

**Study the relationship between phase & line current & voltage of a Delta connected three phase balanced system.**

Submitted To:	Submitted By:
<b>Oishi Jyoti</b> <b>Assistant Professor</b> <b>Dept. Of Electrical &amp; Computer</b> <b>Engineering</b>	Name :Mahmudul Hasan Roll :2210057 Registration :1111 Session :2022-2023 Department of ECE,RUET

# INDEX

<b>SL</b>	<b>Name</b>	<b>Page No</b>
<b>1</b>	<b>Eperiment No</b>	<b>1</b>
<b>2</b>	<b>Experiment Nme</b>	<b>1</b>
<b>3</b>	<b>Objectives</b>	<b>1</b>
<b>4</b>	<b>Required Apparatus</b>	<b>1</b>
<b>5</b>	<b>Theory</b>	<b>1</b>
<b>6</b>	<b>Circuit</b>	<b>1</b>
<b>7</b>	<b>Procedure</b>	<b>2</b>
<b>8</b>	<b>Calculation</b>	<b>2</b>
<b>9</b>	<b>Data Table</b>	<b>2</b>
<b>10</b>	<b>Result</b>	<b>2</b>
<b>11</b>	<b>Discussion</b>	<b>2</b>

## Eperiment No:02

**Name of The Experiment:** Study the relationship between phase & line current & voltage of a Delta connected three phase balanced system.

### Objectives:

1. To learn how to make delta connections.
2. To study the relationship between voltage and current in three phase circuits

### Required Apparatus:

1. Voltmeter
2. Ac Voltage Source
3. Ammeter
4. Resistors
5. Connecting Wires

### Theory:

Within a three-phase system connected by a delta, the relationship between the line and phase values is as follows:

$$V_P = V_L$$

$$\text{And } I_P = I_L/\sqrt{3}$$

where  $I_P$  &  $I_L$  represent phase & line current, and  $V_P$  &  $I_L$  represent phase and line voltages, respectively

### Circuit Diagram:

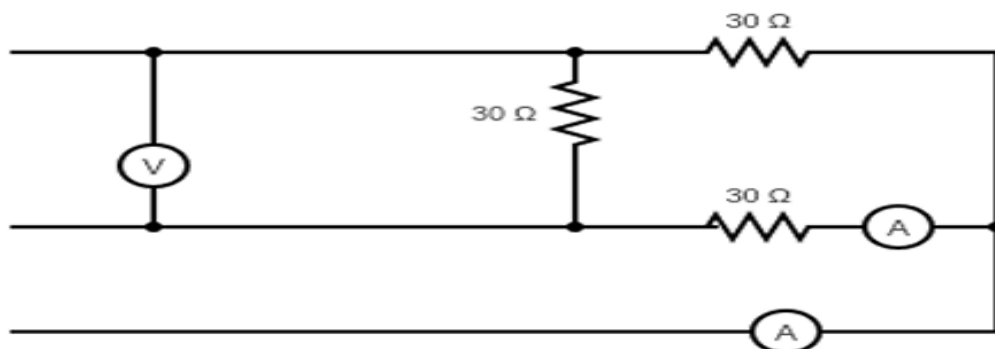


Fig.1: Circuit Diagram

### Procedure:

1. Using the necessary components, a circuit was built by following the circuit diagram.
2. The ammeter and voltmeter were connected according to the diagram.
3. Voltmeter and ammeter readings were recorded into a data table, and an error calculation was made.

### Calculation:

For the 1st one:

$$I_L = 1.5 \text{ A}, I_P(c) = I_L / 3 = 0.86 \text{ A}, I_P(m) = 0.8 \text{ A}, \text{Error} = 6.97\%$$

For the 2nd one:

$$I_L = 2.3 \text{ A}, I_P(c) = I_L / 3 = 1.32 \text{ A}, I_P(m) = 1.2 \text{ A}, \text{Error} = 9.09\%$$

For the 3rd one:

$$I_L = 3.8 \text{ A}, I_P(c) = I_L / 3 = 2.19 \text{ A}, I_P(m) = 2.1 \text{ A}, \text{Error} = 4.11\%$$

For the 4th one:

$$I_L = 4.3 \text{ A}, I_P(c) = I_L / 3 = 2.48 \text{ A}, I_P(m) = 2.3 \text{ A}, \text{Error} = 7.26\%$$

### Data Table:

SL No	V <sub>L</sub>	V <sub>P</sub>	I <sub>P(c)</sub>	I <sub>L</sub>	I <sub>P(m)</sub>	Error(%)
1	40	40	0.86	1.5	0.8	6.97
2	60	60	1.32	2.3	1.2	9.09
3	80	80	2.19	3.8	2.1	4.11
4	100	100	2.48	4.3	2.3	7.26

### Data From Lab:

Data Table:

Roll : 2210055  
2210056  
2210057  
2210058  
2210059  
2210060  
2210061  
2210062

SJ	I <sub>L</sub>	I <sub>Pm</sub>	I <sub>Pc</sub>	V <sub>P</sub>	V <sub>L</sub>	%
1	1.5	0.8	0.86	40	40	6.97
2	2.3	1.2	1.32	60	60	9.09
3	3.8	2.1	2.19	80	80	4.11
4	4.3	2.3	2.48	100	100	7.26

22.0524

**Result:**

From the data table ,we can see that the result is almost same as we expected though it shows some error but that was very small. So it can be said that ,

$$I_p = I_L / \sqrt{3}$$

& line voltage is equal to phase voltage  $V_P = V_L$

**Discussion:**

The experiment successfully verified the relationship between line current and phase current in a balanced, delta-connected three-phase system. The calculated line current roughly matches the values found in theory.