

Heaven's Light is Our Guide



Rajshahi University of Engineering & Technology

Department of Electrical & Computer Engineering

Lab Report

Course Code	ECE 1202
Course Title	Circuit and System Sessional
Date of Submission	01-10-2024

Submitted By:	Submitted To:
Name : Noushin Tabassum	Oishi Jyoti
Roll : 2210058	Assistant Professor
Registration : 1112	Department of Electrical and
Session : 2022-2023	Computer Engineering
Department of ECE, RUET	RUET

Name of the Experiment: Power measurement of three phase balanced system using two wattmeter method.

Theory: The two-wattmeter method is a practical technique used to measure power in a three-phase balanced system. It works by placing two wattmeters across two of the three phases, each connected between one phase and the common neutral or third phase. The total power is determined by summing the readings of both wattmeters, where each wattmeter measures the power in its respective phase. In a balanced system, the sum of the wattmeter readings equals the total real power, and their difference provides information about reactive power.

Circuit diagram:

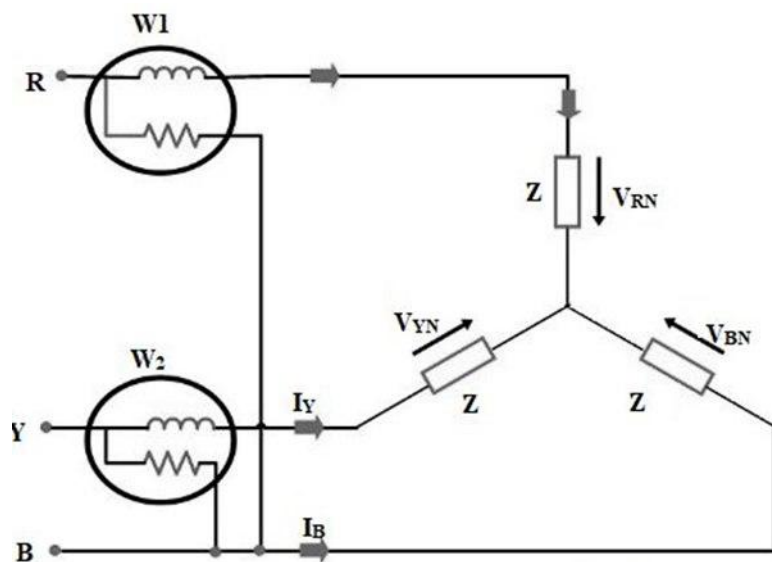


Fig : 3 phased balanced system using two wattmeter method

Required Apparatus:

- 1) Supply
- 2) Variac
- 3) Resistor
- 4) Voltmeter / multimeter
- 5) Ammeters or clamp of Ammeter
- 6) Wattmeters
- 7) Connecting wires

Data Table:

SL No	P1	P2	P _m =P1+P2	V _L	I _L	P _c = $\sqrt{3}$ V _L I _L	Error(%)
1	22	28	50	72.5	0.53	66.554	24.87
2	28	32	60	79.9	0.609	84.28	28.8
3	36	40	76	87.4	0.666	100.82	24.62
4	45	48	93	94.8	0.726	119.208	21.985
5	50	50	100	98.6	0.73	124.67	19.79

Calculation:

For the 1st one:

$$P_m = P1 + P2 = 22 + 28 = 50 \text{ W}, P_c = \sqrt{3}V_L I_L = \sqrt{3} * 72.5 * 0.53 = 66.554 \text{ W}, \text{ Error} = 24.87\%$$

For the 2nd one:

$$P_m = P1 + P2 = 28 + 32 = 60 \text{ W}, P_c = \sqrt{3}V_L I_L = \sqrt{3} * 79.9 * 0.609 = 84.28 \text{ W}, \text{ Error} = 28.8\%$$

For the 3rd one:

$$P_m = P1 + P2 = 36 + 40 = 76 \text{ W}, P_c = \sqrt{3}V_L I_L = \sqrt{3} * 87.4 * 0.666 = 100.82 \text{ W}, \text{ Error} = 24.62\%$$

For the 4th one:

$$P_m = P1 + P2 = 45 + 48 = 93 \text{ W}, P_c = \sqrt{3}V_L I_L = \sqrt{3} * 94.8 * 0.726 = 119.208 \text{ W}, \text{ Error} = 21.985\%$$

For the 5th one:

$$P_m = P1 + P2 = 50 + 50 = 100 \text{ W}, P_c = \sqrt{3}V_L I_L = \sqrt{3} * 98.6 * 0.73 = 124.67 \text{ W}, \text{ Error} = 19.79\%$$

Conclusion:

In conclusion, the two-wattmeter method effectively measures the total power in a three-phase balanced system. By connecting two wattmeters between different phase pairs, the sum of their readings gives the total real power, while the difference provides information about the reactive power. This method is advantageous because it works for both balanced and unbalanced loads and does not require access to the neutral wire. The experiment demonstrates the accuracy and simplicity of the two-wattmeter method, making it widely applicable in practical power measurement scenarios.