

# INDEX

Experiment No	Name of the Experiment
01	Study the relationship between phase voltage and line voltage of a Wye connected 3 phase circuit.
02	Study the relationship between phase current and line current of a Delta connected 3 phase circuit.
03	Study of the power measurement of a three phase balanced system using two wattmeter method.
04	Three phase sequence test using motor.
05	Three phase sequence test using bulbs.