

Heaven's Light is Our Guide



Rajshahi University of Engineering & Technology

Department of Electrical & Computer Engineering

Lab report

Course Code : ECE 1202
Course Title : Circuits and Systems-2 Sessional
Date of experiment : 04-06-2024
Date of Submission : 10-09-2024

Submitted To:	Submitted By:
Oishi Jyoti Assistant Professor, Department of ECE, RUET	Name : S. M Sadman Aziz Sifat Roll : 2210029 Registration : 1083 Session : 2022-2023 Department of ECE, RUET

Experiment No. 02:

Study of the relationship between phase current and line current of a delta connected 3-phase balanced system.

Objectives:

To understand and investigate the link between line currents and phase currents in a balanced three-phase delta (Δ) arrangement, as well as to verify the theoretical correlations through experiments.

Theory:

Two conventional arrangements for the three phases (A, B, and C) in an electrical system are Wye (Y) and Delta (Δ). Every phase coil in a Delta (Δ) connection is connected end to end to create a closed loop. Important things to think about are as follows:

Phase Current (I_P): The current that passes through a single phase or a single three-phase system component. The phase currents in a balanced system have the same magnitude but a 120 degree phase difference.

2. Line Current (I_L): The amount of current flowing along each wire joining the three-phase source to the load.

The connection between phase current (I_P) and line current (I_L) in a balanced Delta (Δ) linked system is provided by:

$$I_{\text{line}} = \sqrt{3} \times I_{\text{phase}}$$

$$V_{\text{line}} = V_{\text{phase}}$$

Required Apparatus:

1. Three-phase AC power supply.
2. Delta connected load (resistors).
3. Voltmeter.
4. Connecting wires.
5. Ammeter.
6. VARIAC
7. Multimeter

Circuit Diagram: -

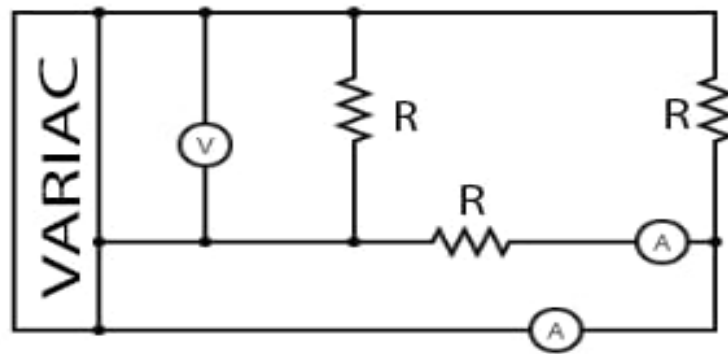


Fig-01: - Delta connection of a 3-phase system.

Data Table: -

SL No	I_L	I_P (Calculated)	I_P (Measured)	V_P	V_L	Error (%)
1	2.25	1.29	1.26	38.3	39.0	2.32
2	0.72	0.41	0.39	12.83	12.84	4.87
3	1.28	0.74	0.7	21.83	22.15	5.4
4	1.87	1.08	1.04	31.6	32.17	3.7
5	2.79	1.61	1.59	47.1	47.3	1.24

Fig-02: - Table from lab

Data Table: $R = 30 \Omega$

SL	I_L	$I_{P \text{ cal}}$	$I_{P \text{ meas}}$	V_P	V_L	% error
1	2.25 2.25	1.29	1.26	37.5 38.3	22.8 39.0	2.32
2	0.72	0.41	0.39	12.83	12.84	4.87
3	1.28	0.74	0.7	21.83	22.15	5.4
4	1.87	1.08	1.04	31.6	32.17	3.7
5	2.79	1.61	1.59	47.1	47.3	1.24

Roll: 19, 22, 24, 26, 28, 29, 30

04.06.24

Result:

As evident from the error calculation, the measured and calculated currents are nearly identical. While there are some minor discrepancies, the values are approximately close. Therefore, it can be concluded that,

$$I_{\text{line}} = \sqrt{3} \times I_{\text{phase}}$$

$$V_{\text{line}} = V_{\text{phase}}$$

Discussion:

Taking into account the tiny margin of error, which might have been caused by either internal or external variables, the experiment can be deemed successful.