

Heaven's Light is Our Guide



Rajshahi University of Engineering & Technology

Department of Electrical & Computer Engineering

Lab Report

Experiment No: 01

Name of the experiment: Study the relationship between phase voltage and line voltage of wye connected 3-phase balanced system.

Course Code	ECE 1202
Course Title	Circuits and Systems-II Sessional
Date of experiment	14-05-2024
Date of Submission	03-09-2024

Submitted By:	Submitted To:
Name : Waliullah	Oishi Jyoti
Roll : 2210035	Lecturer,
Registration : 1089	Department of Electrical &
Session : 2022-2023	Computer Engineering, RUET
Department of ECE, RUET	

Experiment No: 01

Name of the Experiment: Study the relationship between phase voltage and line voltage of wye connected 3-phase balanced system.

1.1 Objective:

To examine and validate the theoretical relationship in a balanced Wye-connected three-phase system between the line and phase voltages.

1.2 Theory:

In a balanced Wye-connected system:

- **Phase Voltage:** The voltage across each individual winding or phase.
- **Line Voltage:** The voltage between any two lines.

The theoretical connection in a Wye connected system is $V_{\text{line}} = \sqrt{3} \cdot V_{\text{ph}}$, which represents the relationship between the line and phase voltages.

Since two phase voltages spaced 120 degrees apart equal the vector sum of the line voltage, this connection results.

1.3 Required Apparatus:

1. Ammeter
2. Voltmeter
3. Resistance
4. AC voltage source
5. Connecting wires
6. Multimeter

1.4 Circuit Diagram:

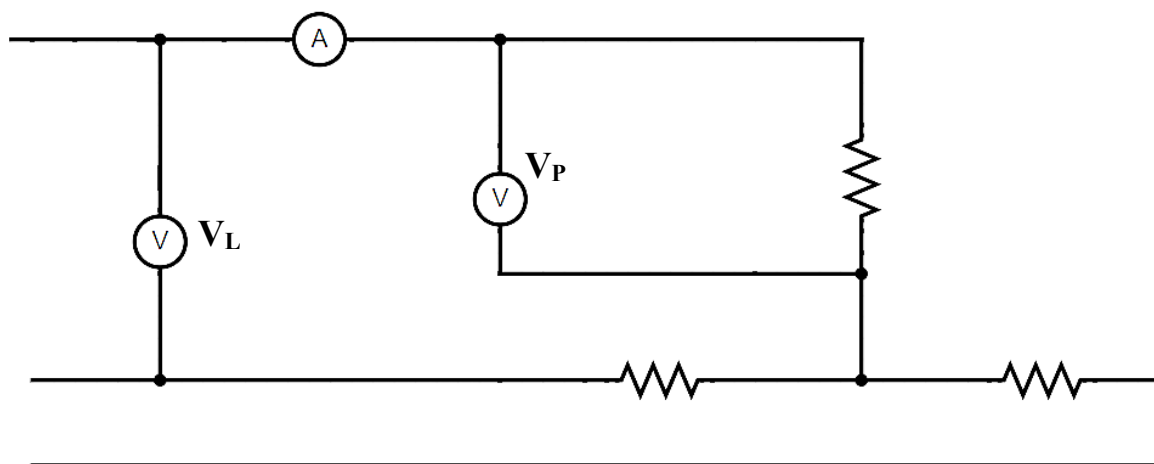


Fig. 1.1: Circuit diagram


1.5 Procedure:

The circuit was built according to the diagram and the readings were collected several times for verification.

1.6 Data Table:

Sl No.	V_L (V)	V_P (m) (V)	V_P (cal) (V)	I_L (A)	I_P (A)	Error(%)
01	98.90	55.80	57.10	0.55	0.55	2.39
02	71.00	39.90	41.00	0.39	0.39	2.75
03	124.50	70.10	71.88	0.70	0.70	2.53

SLNo.	V_L	V_P (m)	V_P (c)	I_L (A)	I_P (A)	Error(%)
1	98.9	55.8	57.1	0.55	0.55	2.39%
2	71	39.9	41	0.39	0.39	2.75%
3	124.5	70.1	71.88	0.70	0.70	2.53%


14.05.21

1.7 Discussion:

The results we had gotten from the experiment were exactly what were anticipated. However, due to few mechanical and mathematical errors, they had not been precise. It had occasionally taken many attempts to finish the experiment because sometimes experiment materials seemed to be faulty and was used by the experimenters incorrectly, which had led to incorrect calculations and results. If everything was flawless, the outcome would be precisely correct as per the theory.

1.8 Precautions:

1. The connections should be made carefully.
2. The AC voltage source should be handled with care maintaining safety measures.
3. The readings of voltmeter and ammeter should be taken as precisely as possible.

1.9 Reference:

- (i) Charles K. Alexandar and Matthew N. O. Sadiku, “Fundamentals of Electric Circuit”, 5th Edition, 1221 Avenue of the Americas, New York
- (ii) Wikipedia